

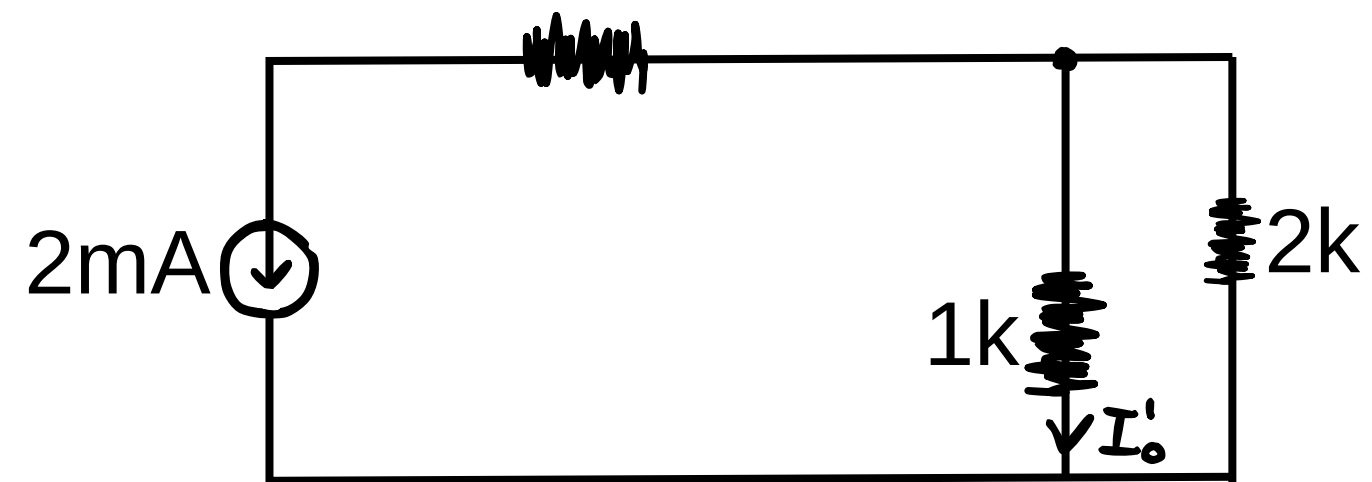


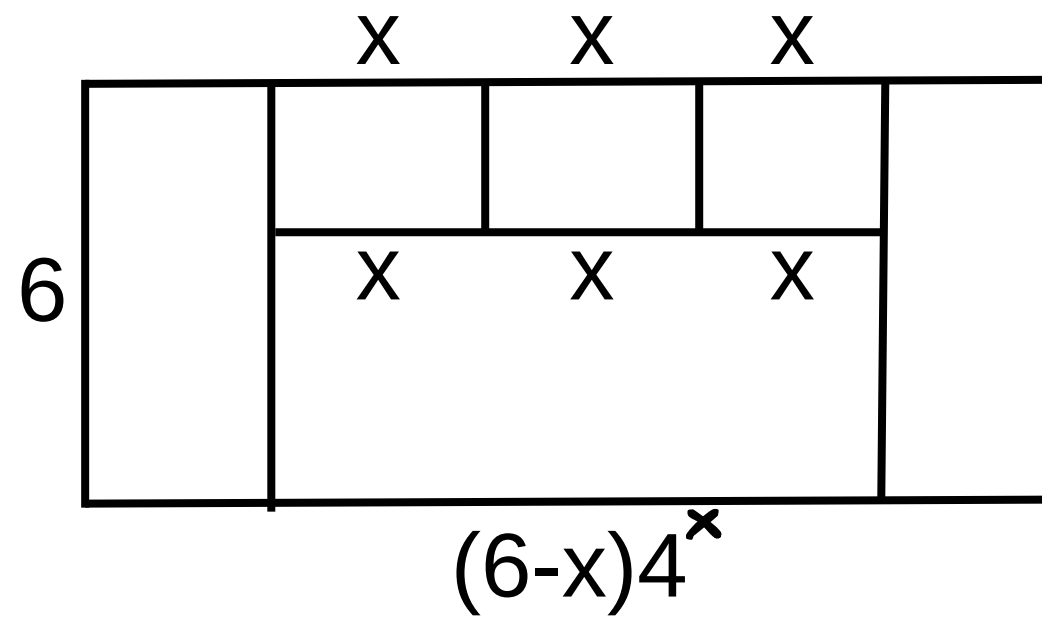

$$I_o' = \frac{V}{R} = \frac{\frac{4}{3}}{1k} = \frac{4}{3} \text{ mA} \uparrow$$

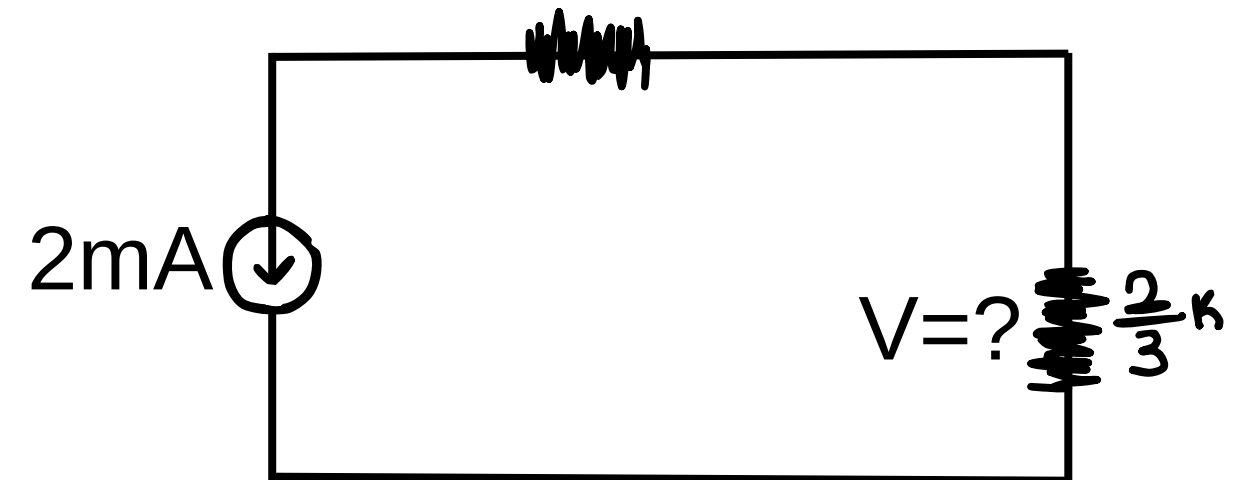
$$\boxed{\frac{4}{3} = \text{mA} \downarrow}$$




$$V = I \cdot R = 2\text{mA} \cdot \frac{2}{3}k\Omega = \frac{4}{3}V$$


$$I_o' = 2 \cdot \frac{2k}{1k\Omega + 2k} = \frac{4}{3}k \uparrow$$
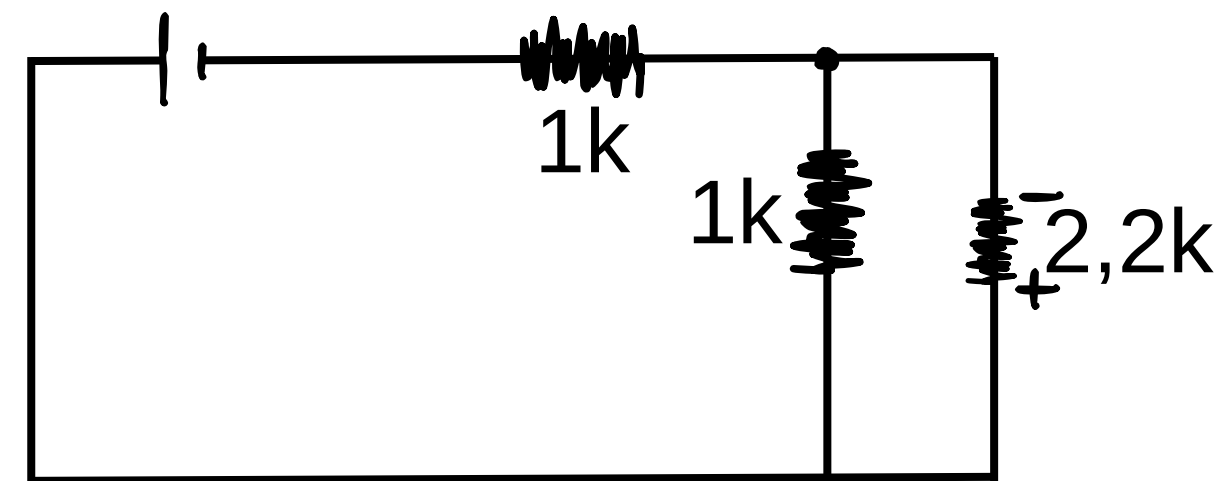
$$\boxed{I_o' = -\frac{4}{3}k \downarrow}$$



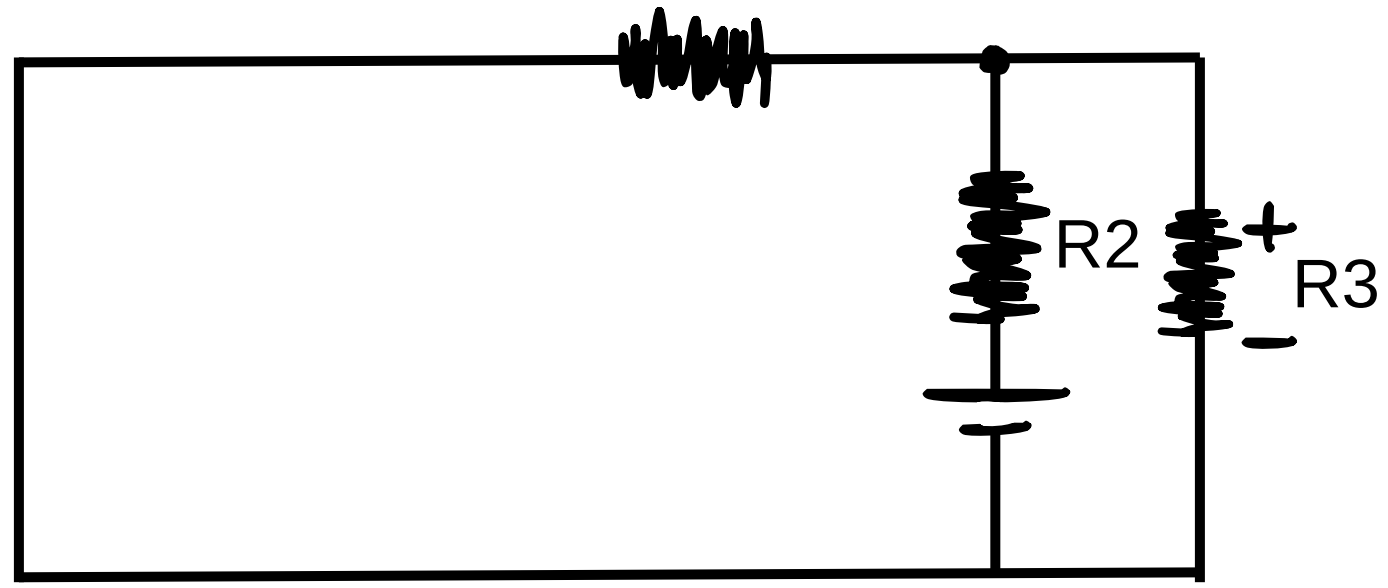
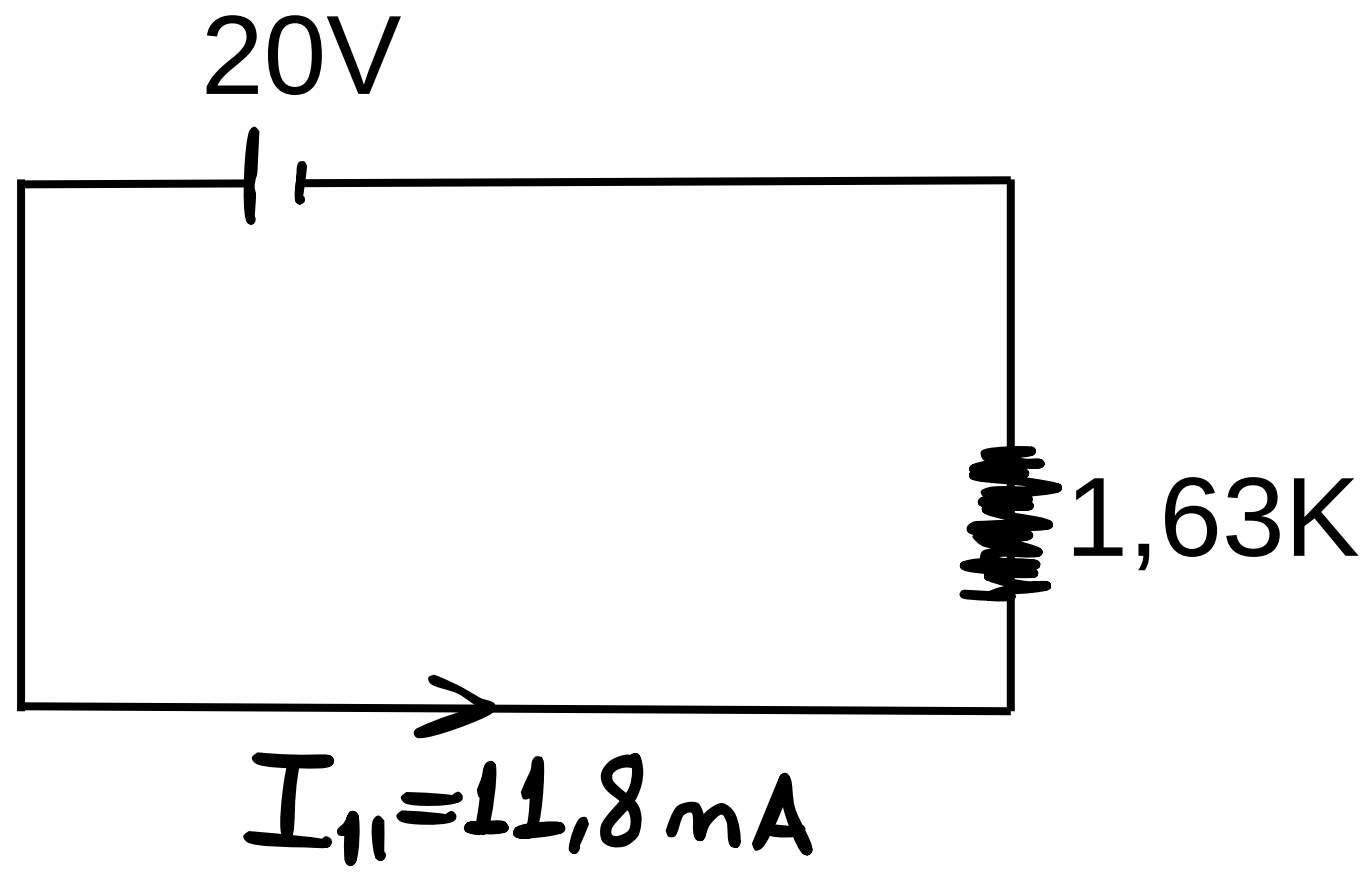
$$I'_o = 10 \cdot \frac{4}{1+4} = \frac{40}{5} = 8 \text{ mA}$$



9. HAFTA